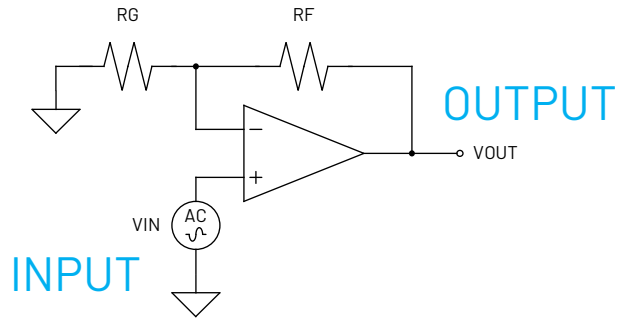


Demystifying Noise – KWIK Labs


Ed Mullins, Principal Applications Engineer

Total Integrated Noise KWIK Lab Step-by-Step Guide


Estimate the Noise



1. Start with your circuit

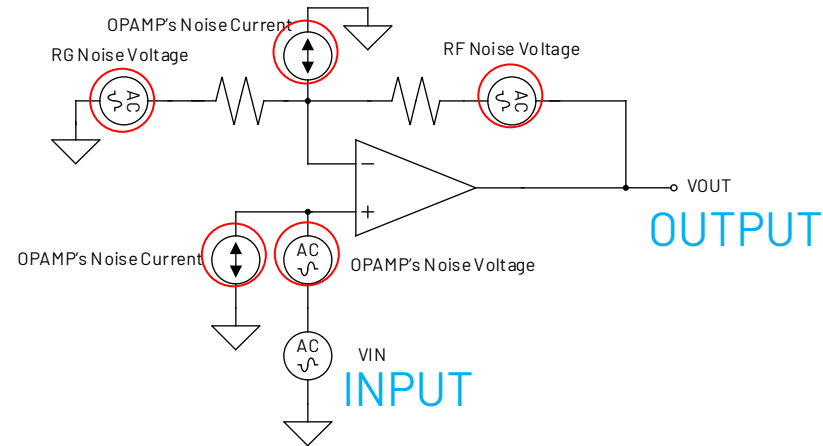

2. Add the noise sources

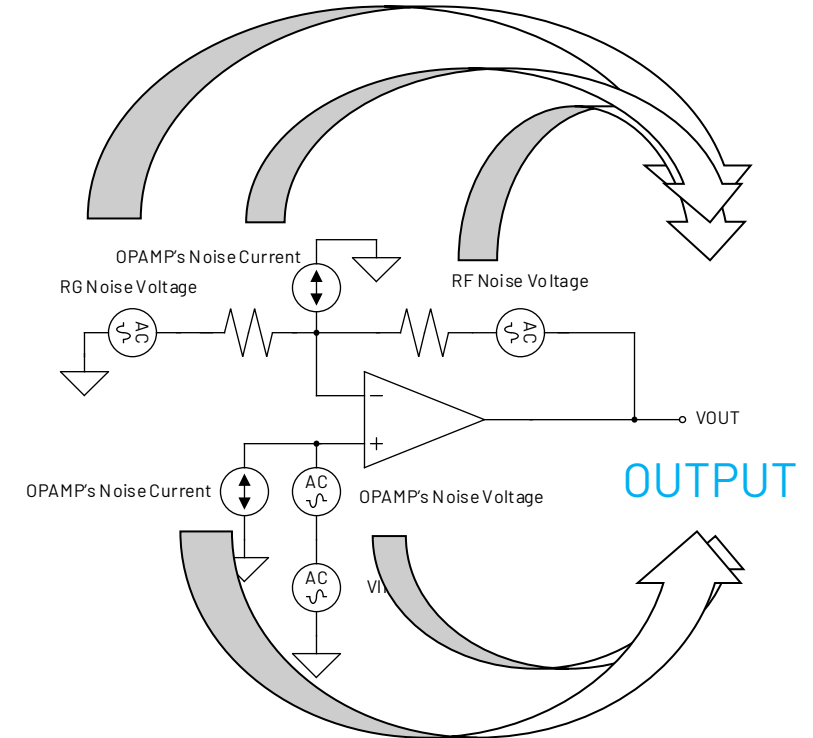

3. Refer the noise sources to the output


Noise Bandwidth and Noise Sources

► Identify the noise Bandwidth

- ADA4510 configured in $G = 1001$
 - Small-signal bandwidth = $10.4\text{MHz}/1001 = 10.4\text{kHz}$
 - Noise bandwidth = $10.4\text{kHz} * 1.57 = 16.3\text{kHz}$


► Identify each noise source:

- $R_g = 1\text{k} \rightarrow 4\text{nV}/\sqrt{\text{Hz}}$
- $R_f = 1\text{M} \rightarrow 127\text{nV}/\sqrt{\text{Hz}}$
- $R_s = 1\text{M} \rightarrow 127\text{nV}/\sqrt{\text{Hz}}$
- ADA4510 $\rightarrow V_n = 5\text{nV}/\sqrt{\text{Hz}} (@16.3\text{kHz})$
- ADA4510 $\rightarrow I_{n-} = 200\text{fA}/\sqrt{\text{Hz}} (@16.3\text{kHz})$
- ADA4510 $\rightarrow I_{n+} = 200\text{fA}/\sqrt{\text{Hz}} (@16.3\text{kHz})$

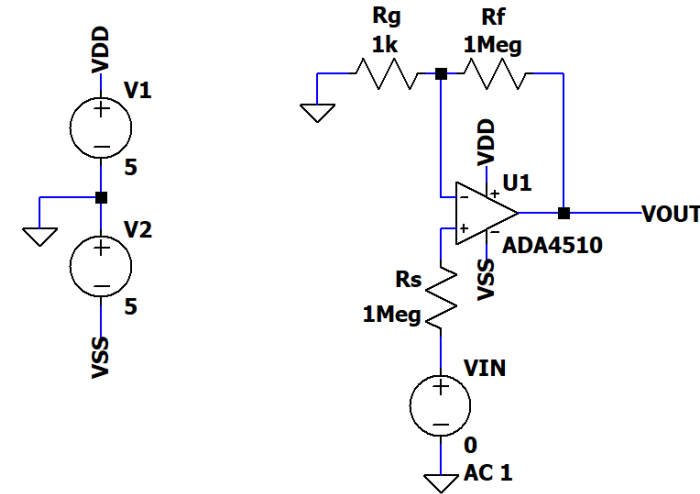

► Refer each Noise Source to the Output:

- $R_g = 1k \rightarrow 4nV/\sqrt{Hz} * 1000 = 4\mu V/\sqrt{Hz} (RTO)$
- $R_f = 1M \rightarrow 127nV/\sqrt{Hz} * 1 = 127nV/\sqrt{Hz} (RTO)$
- $R_s = 1M \rightarrow 127nV/\sqrt{Hz} * 1001 = 127\mu V/\sqrt{Hz} (RTO)$
- ADA4510 $\rightarrow V_n = 5nV/\sqrt{Hz} (@16.3kHz) * 1001 = 5\mu V/\sqrt{Hz} (RTO)$
- ADA4510 $\rightarrow I_{n-} = 200fA/\sqrt{Hz} (@16.3kHz) * 1M = 200nV/\sqrt{Hz} (RTO)$
- ADA4510 $\rightarrow I_{n+} = 200fA/\sqrt{Hz} (@16.3kHz) * 1M * 1001 = 200\mu V/\sqrt{Hz} (RTO)$

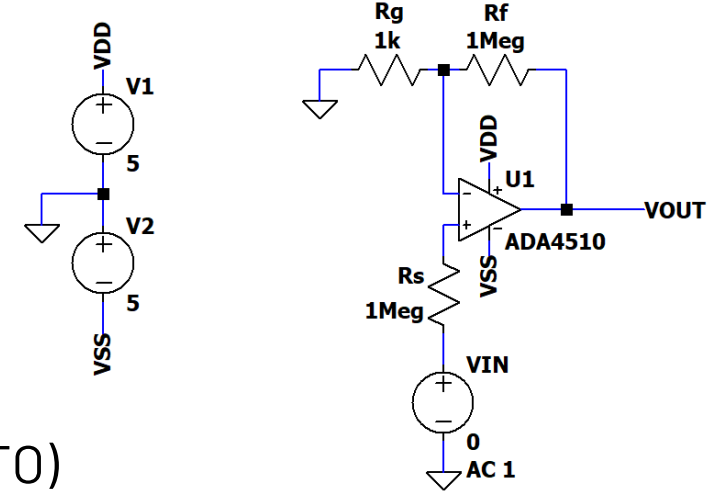

Sum the NSD at the output:


$$V_{OUT_{NSD@16.3kHz}} = \sqrt{\left(4\mu V / \sqrt{Hz}\right)^2 + \left(127nV / \sqrt{Hz}\right)^2 + \left(127\mu / \sqrt{Hz}V\right)^2 + \left(5\mu V / \sqrt{Hz}\right)^2 + \left(200nV / \sqrt{Hz}\right)^2 + \left(200\mu V / \sqrt{Hz}\right)^2} = 237\mu V / \sqrt{Hz}$$

Estimate the Total Noise:

$$V_{OUT_{TOTALNOISEV_{PP}}} = 6.6 \times 237\mu V / \sqrt{Hz} \times \sqrt{16.3kHz} = 200mV_{PP}$$



Identify Dominant Noise Sources

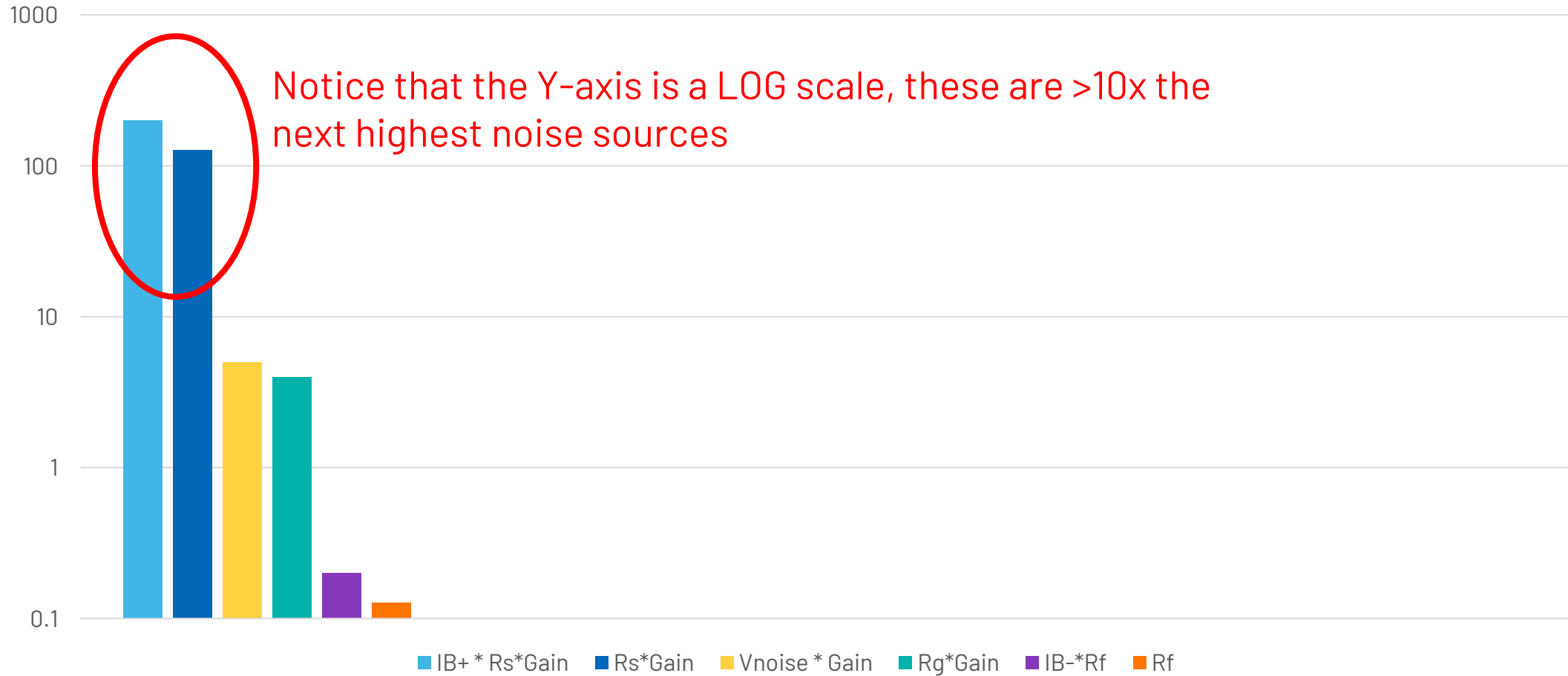Output Noise Spectral Density Pareto Chart




Simulating Noise in LTSpice


- ▶ Add the .noise command as a SPICE directive with the listed arguments:
 - Output: The **node** where you want to examine the **output referred noise**
 - Input: The **source** where you want to examine the **input referred noise**
 - Type of sweep: octave, decade, linear or list
 - Number of points: per octave, per decade, etc
 - Start Frequency: Lowest frequency in the sweep in Hz
 - Stop Frequency: Highest frequency in the sweep in Hz

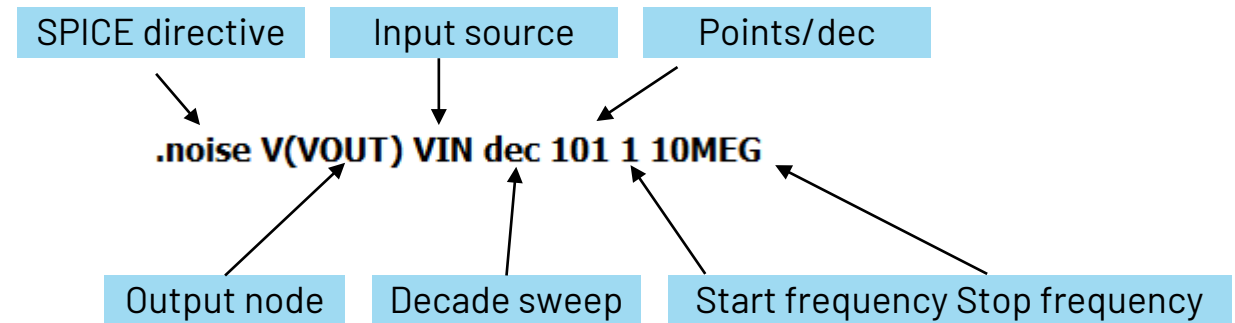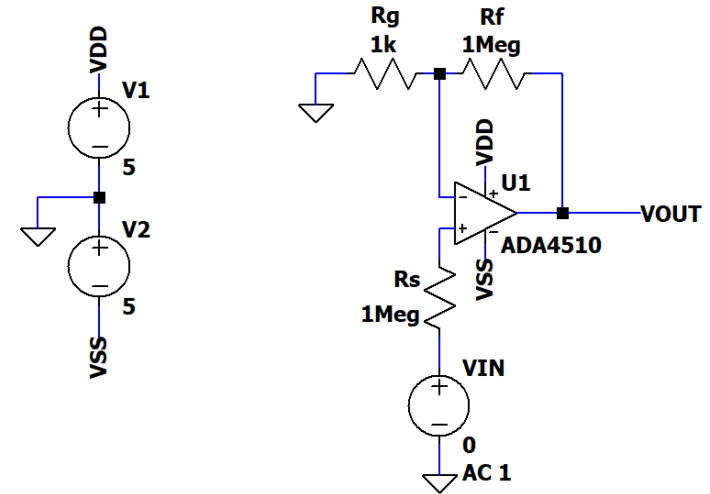

Simulating Noise in LTSpice

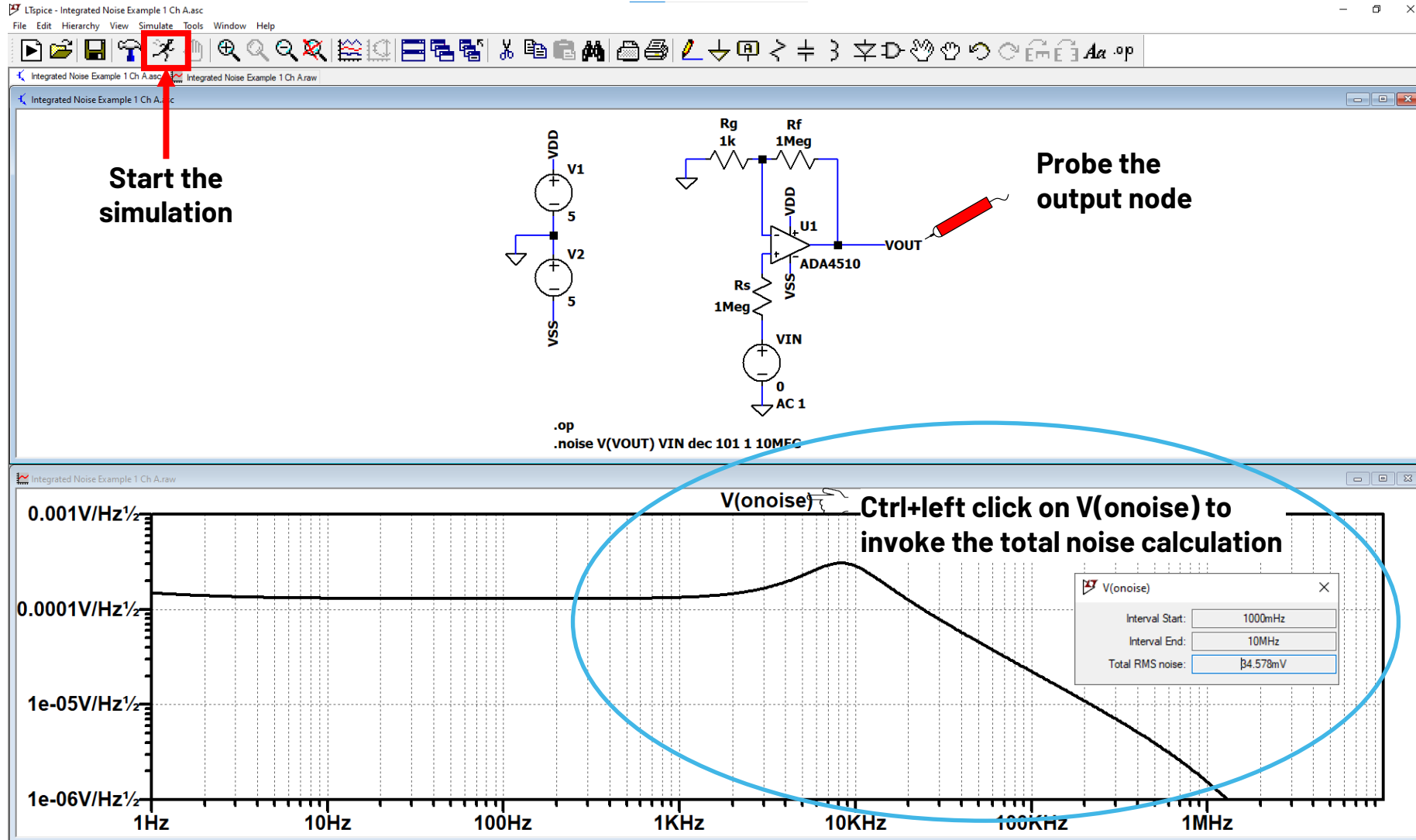


Output Referred Noise Spectral Density


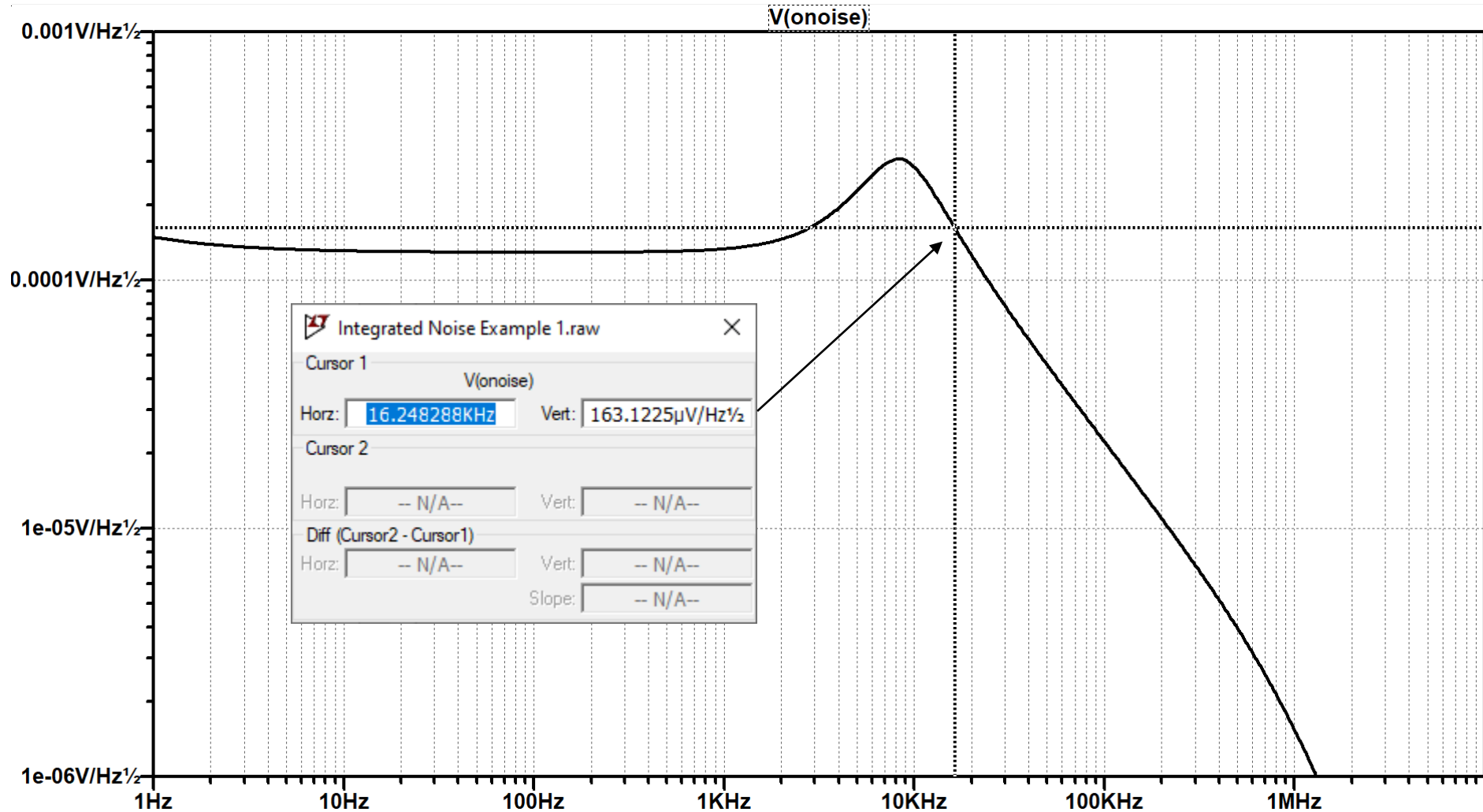


- ▶ Place the cursor at the noise bandwidth of 16.3kHz
- ▶ We estimated $237\mu V/\sqrt{Hz}$ at the noise bandwidth of 16.3 kHz
- ▶ This is slightly past the $-3dB$ point
- ▶ Calculating $\sim 3dB$ down from our estimate we would expect $167\mu V/\sqrt{Hz}$
- ▶ The simulation shows $163\mu V/\sqrt{Hz}$

Total Noise

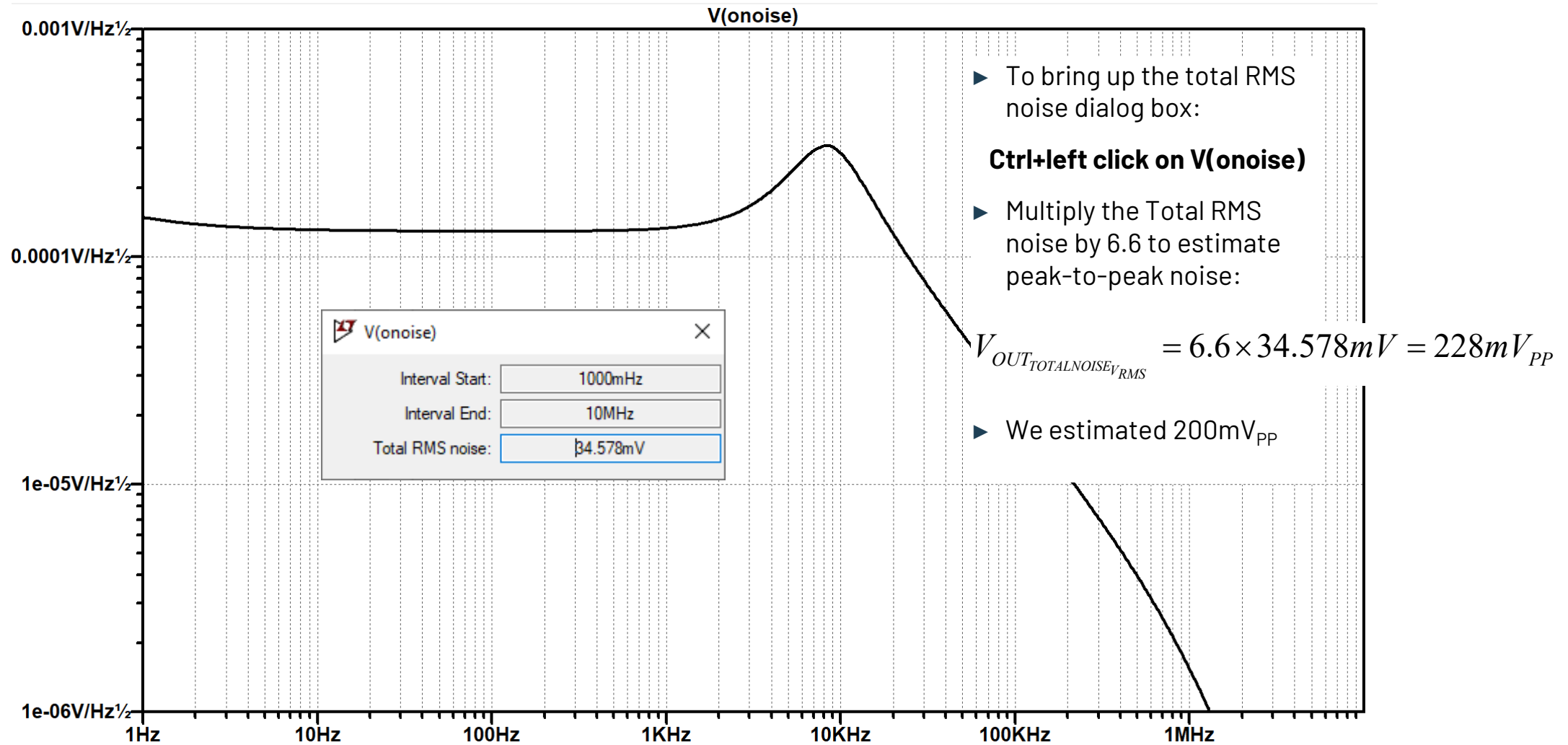

Integrated Noise Demo Board Schematic

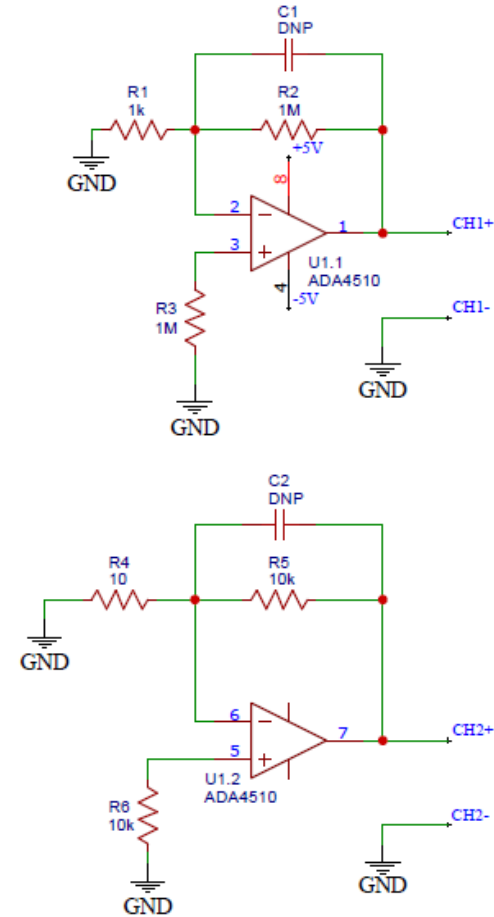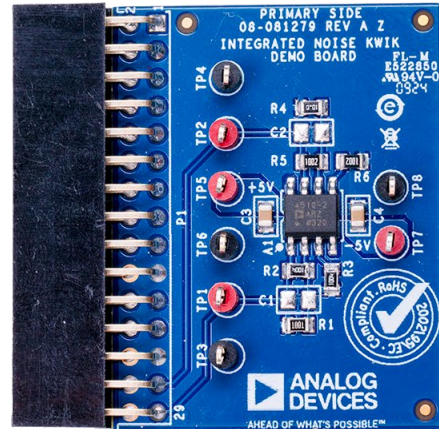

Physically Connect PCB to ADALM2k



Using EVAL-KW4501Z


Carefully align pins and insert firmly

ADALM2000 should be powered off when connecting or disconnecting the PCB

Launch Scopy and Load Config File

- ▶ Connect the ADALM2000 to your laptop and launch Scopy
- ▶ Click on the M2K icon
- ▶ Click connect
- ▶ Once connected click on load and load the file named:

"Integrated Noise Scopy Config Ch A.ini"

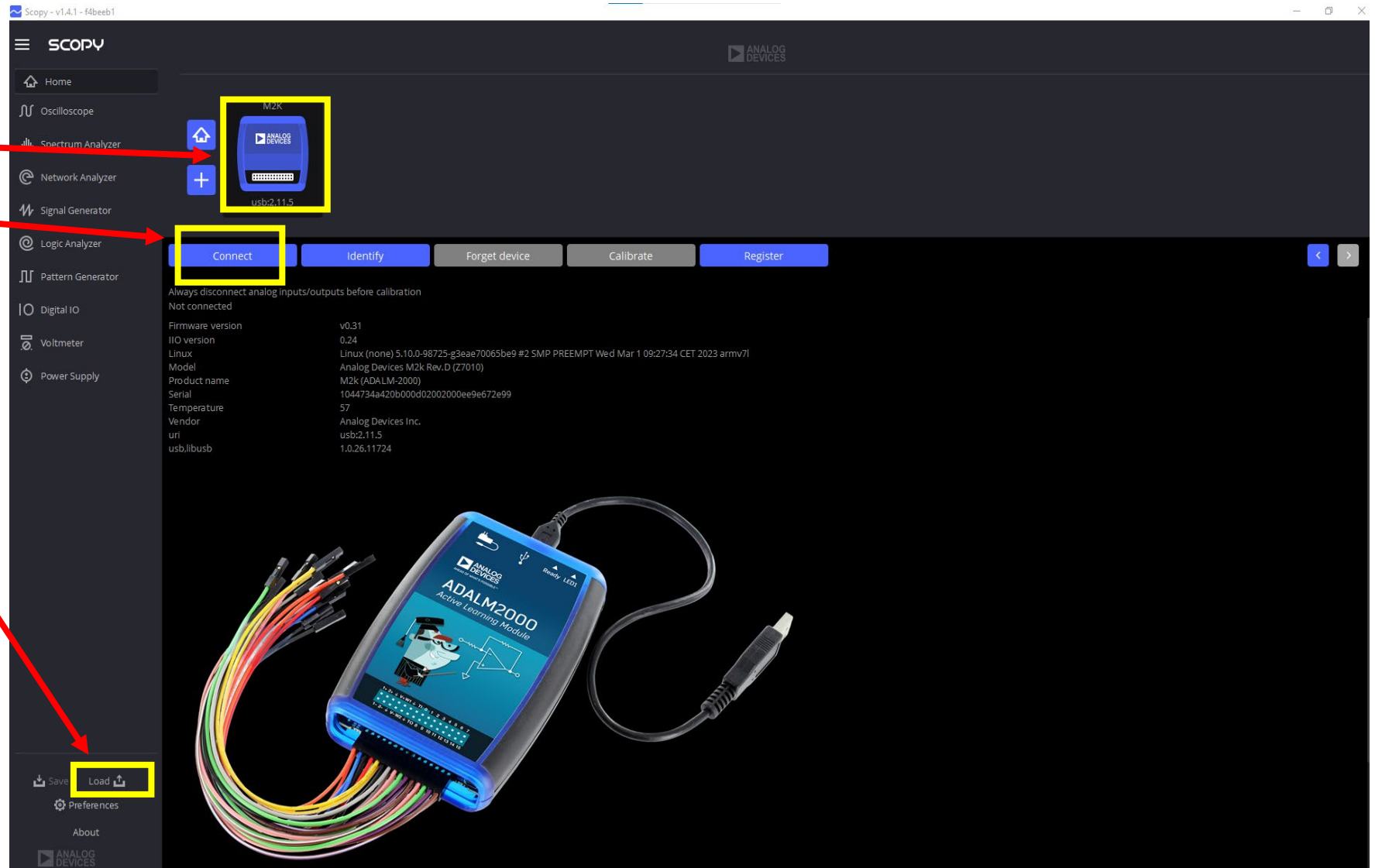

Let's Have a Look at the Total Noise

- ▶ Click "Run" to start the oscilloscope




Review the Result...is it about what you expected?



- ▶ You can click the **stop button** and look at the **peak-to-peak measurement**
- ▶ Try running and stopping a few times...you will notice some variation in the result...this is the nature of noise
- ▶ If your result seems too high, you might be picking up external noise (the circuit has very high impedances and is in a high gain) try moving the board or rotating it to reduce any external interference 😊

Reducing the Noise

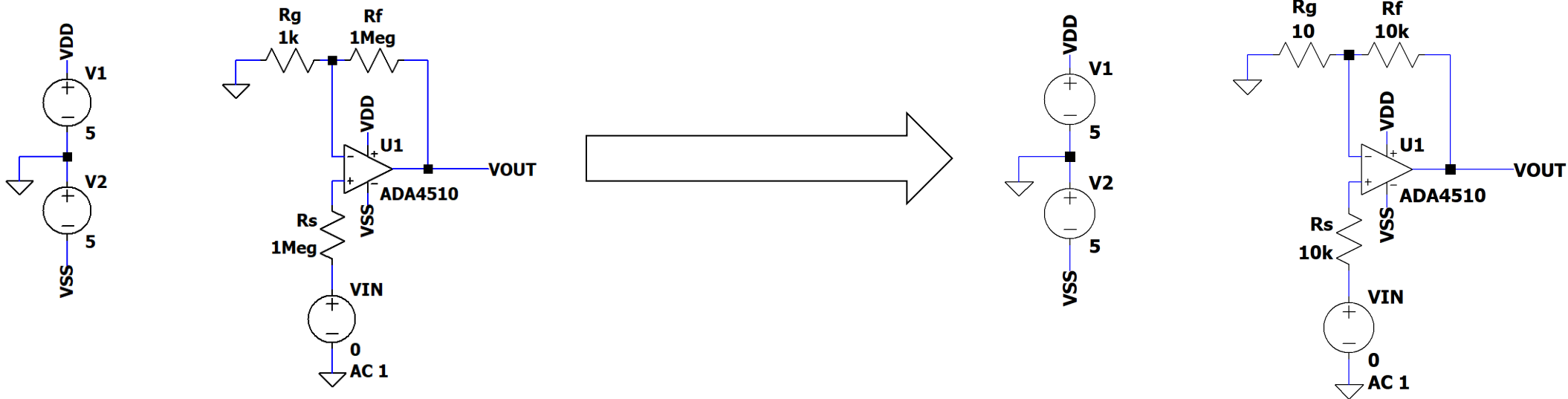- ▶ In the previous example we saw that the dominant sources of noise were the I_{B+} noise current multiplied by the source impedance multiplied by the gain and the voltage noise of the source resistance multiplied by the gain
- ▶ Let's reduce all the impedance values by 100, keeping the same gain, but with less noise contribution from I_{B+} and R_s




Example for a Simple Non-Inverting Amplifier

► Identify the noise Bandwidth

- ADA4510 configured in $G = 1001$
 - Small-signal bandwidth = $10.4\text{MHz}/1001 = 10.4\text{kHz}$
 - Noise bandwidth = $10.4\text{kHz} * 1.57 = 16.3\text{kHz}$

► Identify each noise source:



- $R_g = 10 \rightarrow 0.4\text{nV}/\sqrt{\text{Hz}}$
- $R_f = 10\text{k} \rightarrow 12.7\text{nV}/\sqrt{\text{Hz}}$
- $R_s = 1\text{k} \rightarrow 12.7\text{nV}/\sqrt{\text{Hz}}$
- ADA4510 $\rightarrow V_n = 5\text{nV}/\sqrt{\text{Hz}} (@16.3\text{kHz})$
- ADA4510 $\rightarrow I_{n-} = 200\text{fA}/\sqrt{\text{Hz}} (@16.3\text{kHz})$
- ADA4510 $\rightarrow I_{n+} = 200\text{fA}/\sqrt{\text{Hz}} (@16.3\text{kHz})$

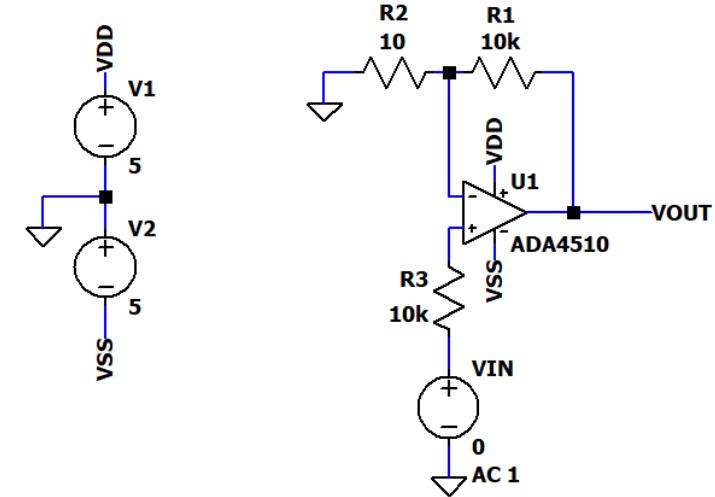

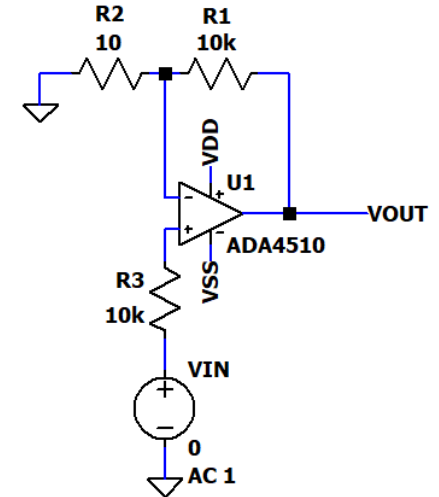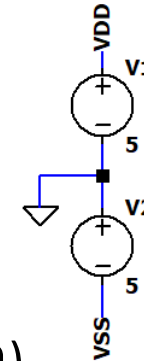Example for a Simple Non-Inverting Amplifier

► Refer each Noise Source to the Output:

- $R_g = 10 \rightarrow 0.4\text{nV}/\sqrt{\text{SQRT-Hz}} \times 1000 = 0.4\mu\text{V}/\sqrt{\text{SQRT-Hz}} (\text{RTO})$
- $R_f = 10\text{k} \rightarrow 12.7\text{nV}/\sqrt{\text{SQRT-Hz}} \times 1 = 12.7\text{nV}/\sqrt{\text{SQRT-Hz}} (\text{RTO})$
- $R_s = 10\text{k} \rightarrow 12.7\text{nV}/\sqrt{\text{SQRT-Hz}} \times 1001 = 12.7\mu\text{V}/\sqrt{\text{SQRT-Hz}} (\text{RTO})$
- ADA4510 $\rightarrow V_n = 5\text{nV}/\sqrt{\text{SQRT-Hz}} (@16.3\text{kHz}) \times 1001 = 5\mu\text{V}/\sqrt{\text{SQRT-Hz}} (\text{RTO})$
- ADA4510 $\rightarrow I_{n-} = 200\text{fA}/\sqrt{\text{SQRT-Hz}} (@16.3\text{kHz}) \times 10\text{k} = 2\text{nV}/\sqrt{\text{SQRT-Hz}} (\text{RTO})$
- ADA4510 $\rightarrow I_{n+} = 200\text{fA}/\sqrt{\text{SQRT-Hz}} (@16.3\text{kHz}) \times 10\text{k} \times 1001 = 2\mu\text{V}/\sqrt{\text{SQRT-Hz}} (\text{RTO})$



Sum the NSD at the output:

$$V_{OUT_{NSD@16.3kHz}} = \sqrt{(0.4\mu\text{V} / \sqrt{\text{Hz}})^2 + (12.7\text{nV} / \sqrt{\text{Hz}})^2 + (12.7\mu\text{V} / \sqrt{\text{Hz}})^2 + (5\mu\text{V} / \sqrt{\text{Hz}})^2 + (2\text{nV} / \sqrt{\text{Hz}})^2 + (2\mu\text{V} / \sqrt{\text{Hz}})^2} = 14\mu\text{V} / \sqrt{\text{Hz}}$$


Estimate the Total Noise:

$$V_{OUT_{TOTALNOISEV_{PP}}} = 6.6 \times 14\mu\text{V} / \sqrt{\text{Hz}} \times \sqrt{16.3\text{kHz}} = 12\text{mV}_{PP}$$

Load Config File


- ▶ Load the file named:

"Integrated Noise Scopy Config Ch B.ini"

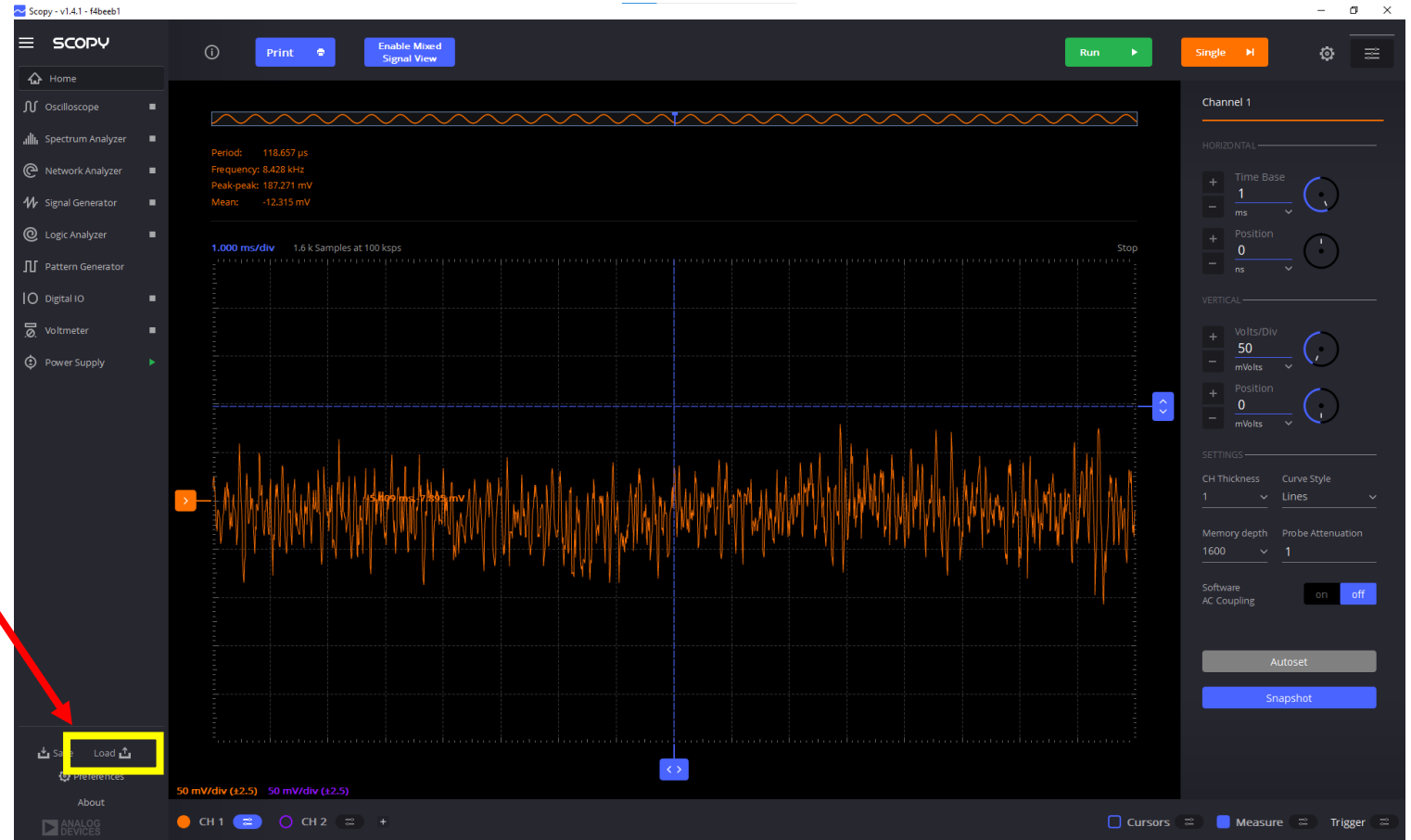

Let's Have a Look at the Total Noise


► Click "Run" to start the oscilloscope

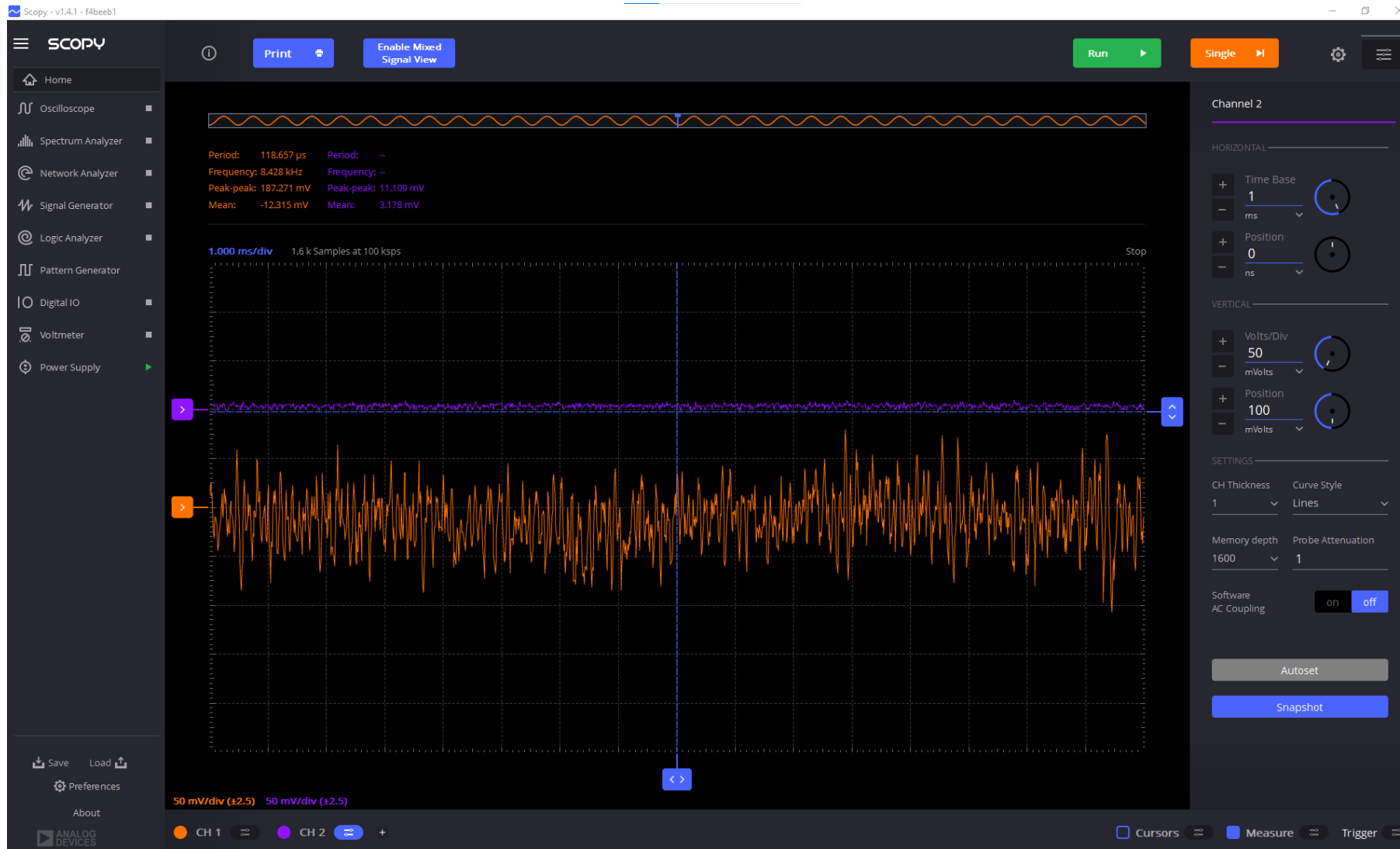

- Click "Run" to start the oscilloscope
- Notice both Ch1 and Ch2 are on the same scale
- You see how much the noise is reduced

Let's Zoom In and Measure

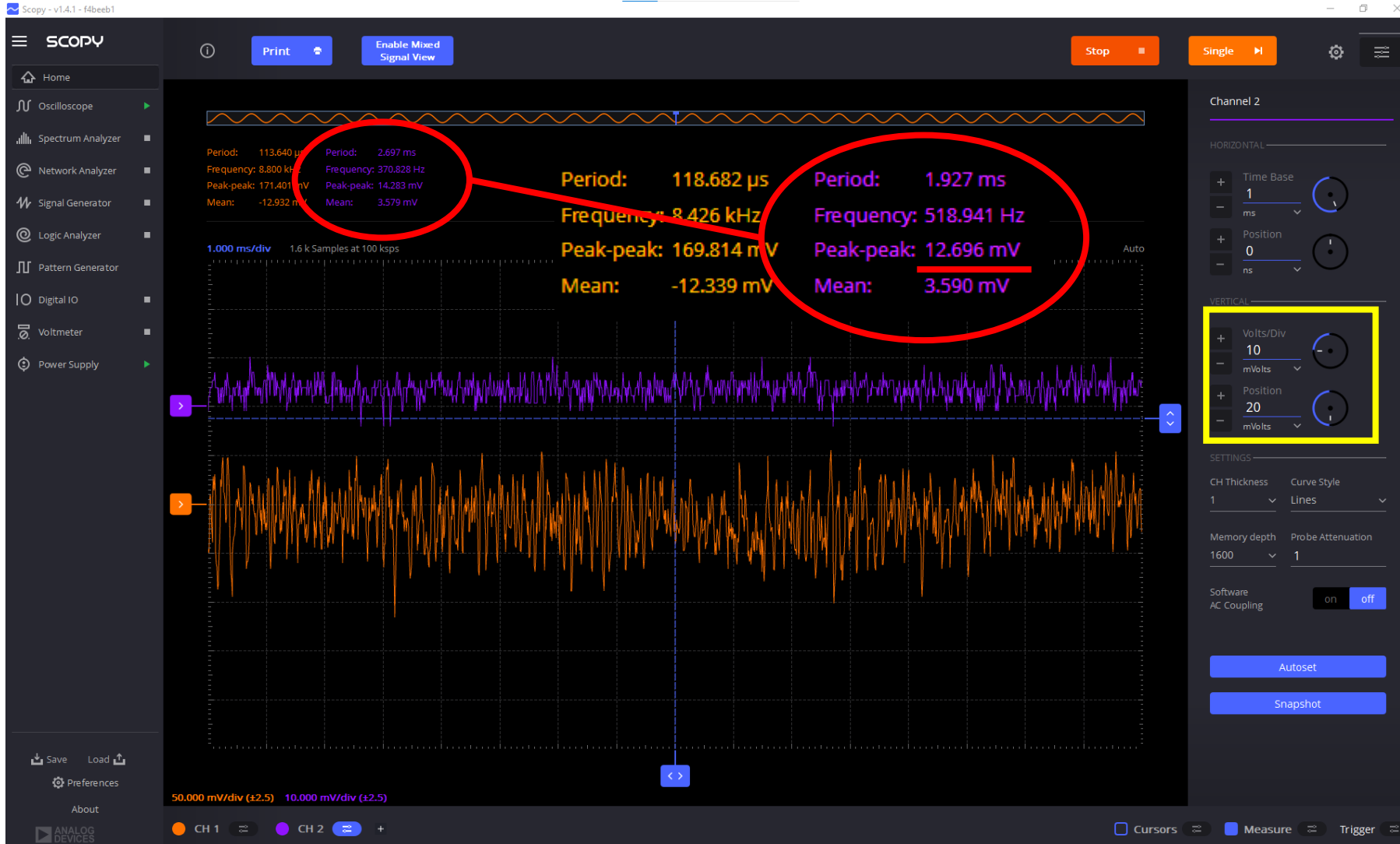
- ▶ Click "Run" to start the oscilloscope




- ▶ Change Ch 2 to 10mV/Div
- ▶ Change Ch2 Position to 20mV
- ▶ Measure the peak-to-peak noise

Shutting Down

Shutting Down

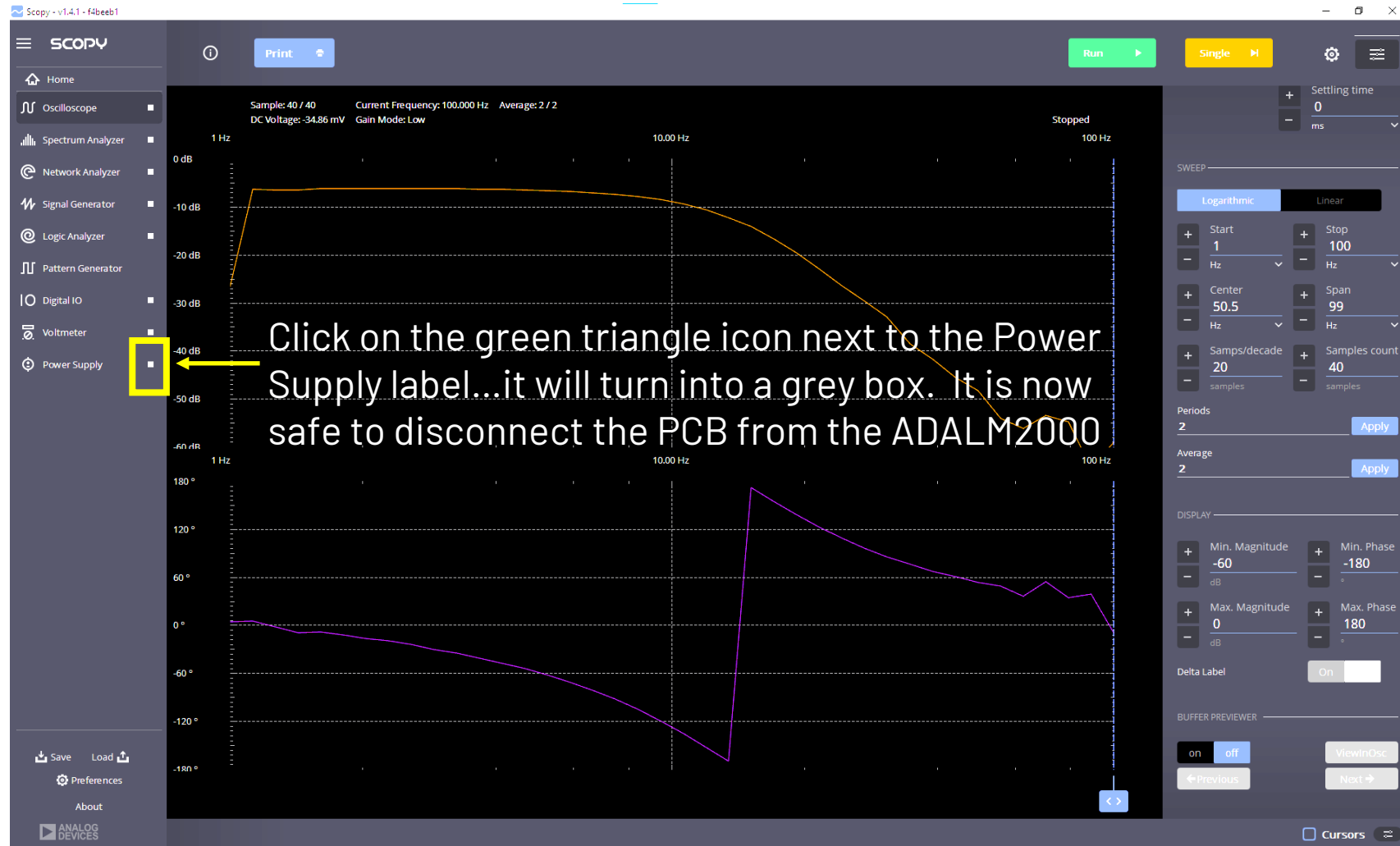

Shutting Down

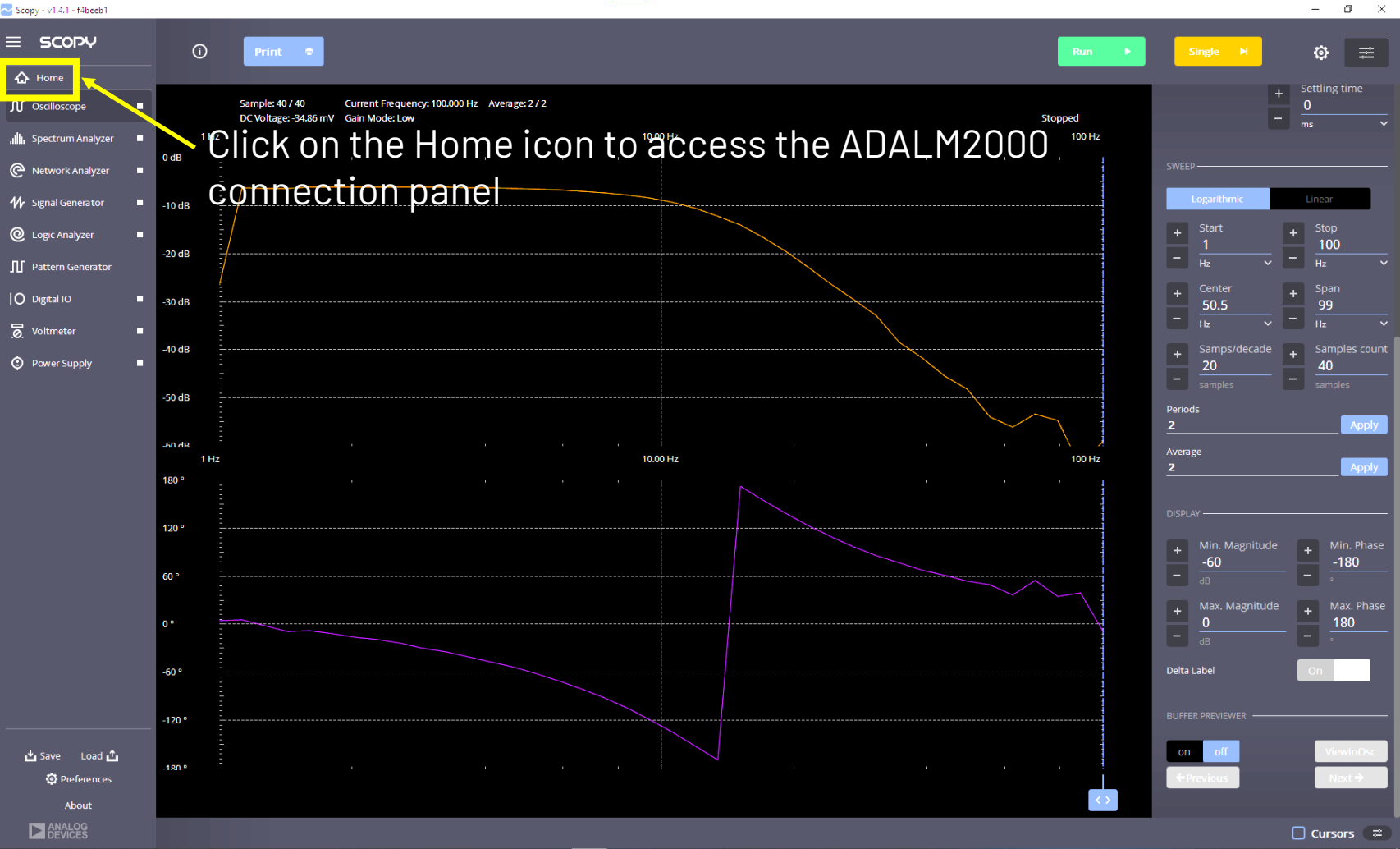

Click on the Disconnect Button



Scopy - v1.4.1 - f4beeb1

SCOPE

Home

Oscilloscope

Spectrum Analyzer

Network Analyzer

Signal Generator

Logic Analyzer

Pattern Generator

Digital IO

Voltmeter

Power Supply

Disconnect Identify Forget device Calibrate Register

Always disconnect analog inputs/outputs before calibration

Calibrated

Connected

Firmware version v0.3

I/O version 0.24

Linux (none) 5.10.0-08725-g3aa70065be9 #2 SMP PREEMPT Wed Mar 1 09:27:34 CET 2023 armv7l

Model Analog Device (ADALM2000)

Product name M2k (ADALM2000)

Serial 1044734a420b00d02002000ee9e672e99

Temperature 61.4

Vendor Analog Devices

uri usb2.28.5

usb.libusb 1.0.26.11724

Save Load

Preferences

About

ANALOG DEVICES

ADALM2000 Active Learning Module

Thank You!